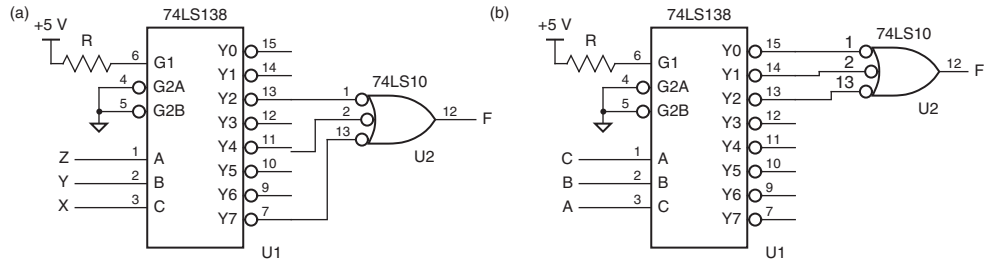


3e5.19 6.207



3e5.35 6.218 With the stated input combination, Y5_L is LOW and the other outputs are HIGH. We have the following cases:

- (a) Negating G2A_L or G2B_L causes Y5_L to go HIGH within 18 ns.
- (b) Negating G1 causes Y5_L to go HIGH within 26 ns.
- (c) Changing A or C causes Y5_L to go HIGH within 27 ns (the change propagates through 3 levels of logic internally), and causes Y4_L or Y1_L respectively to go LOW within 41 ns (2 levels).
- (d) Changing B causes Y5_L to go HIGH within 20 ns (2 levels), and causes Y7_L to go LOW within 39 ns (3 levels). The delays in the 'LS138 are very strange—the worst-case t_{pHL} for 3 levels is shorter than for 2 levels!

3e5.80 6.231

